

Light Emitting Diode(LED)

An LED is a simple electronic component that emits light when current passes through it. LEDs are widely used in electronics projects as indicators or signals to show the status of a system.

LED Pin Configuration:

Anode (+): The longer pin, which connects to the positive side (5V or output pin of Arduino).

Cathode (-): The shorter pin, which connects to the negative side (GND).

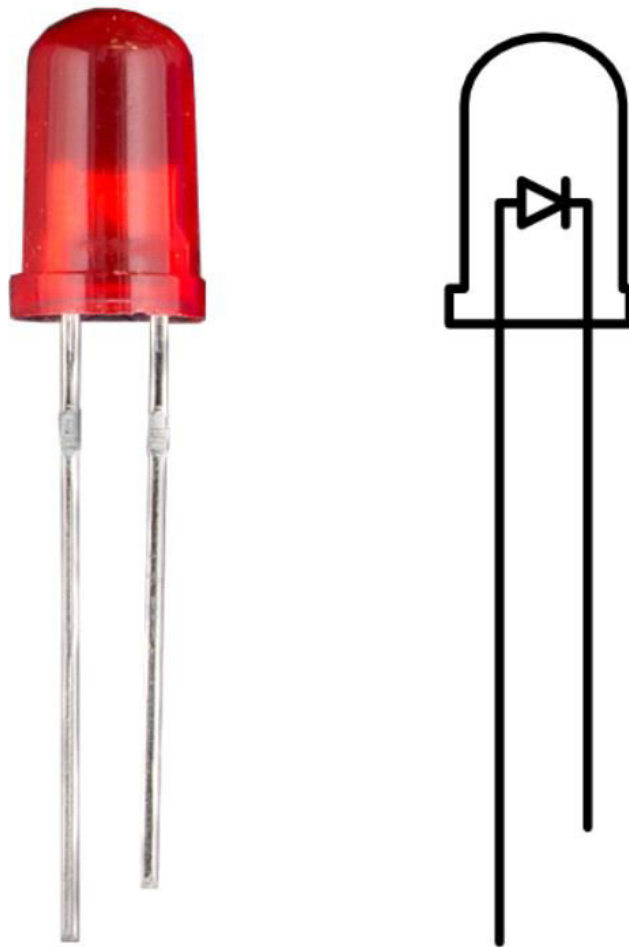


Fig1:Light

Emitting Diodes

How to Use an LED with Arduino:

We can control an LED by connecting it to any digital pin of the Arduino and using the `digitalWrite()` function to turn it on or off.

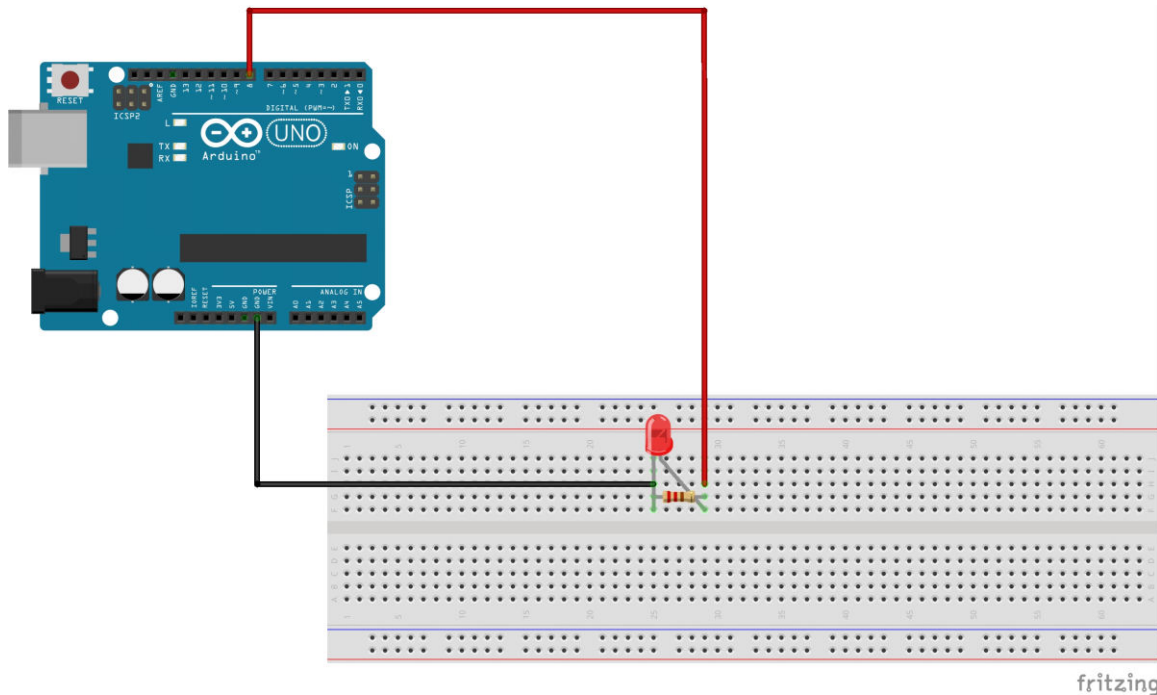


Fig2:LED with

Arduino

Current-Limiting Resistor:

Always use a current-limiting resistor (typically 220Ω to $1K\Omega$) in series with the LED to prevent it from burning out due to excessive current. The resistor ensures that the current passing through the LED stays within safe limits.

Applications:

Status Indicators: LEDs are used to show whether a system is active or idle.

Visual Feedback: In interactive projects, LEDs provide

immediate visual feedback for user input.

Light Displays: Arrays of LEDs are used in displays, decorative lights, and patterns.